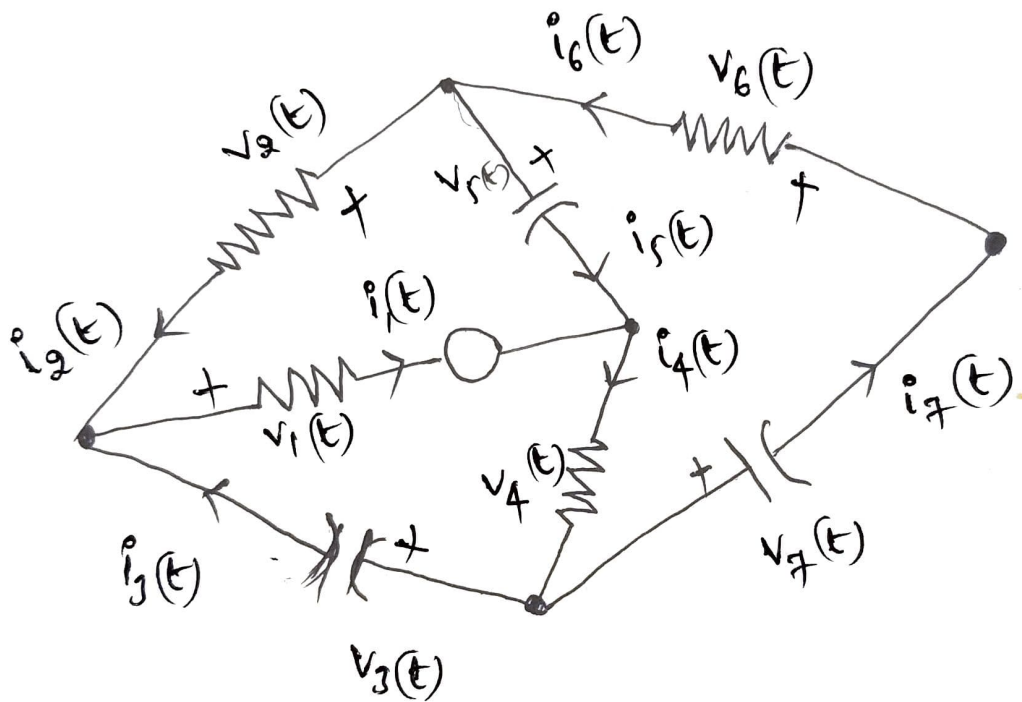



# Electrical Network Analysis by GRAPH THEORY

Let  $G$  be a connected directed graph of 'e' edges and 'n' vertices, representing an electrical network.



The digraph representation of this electrical network is given as follows:

Fig(1):

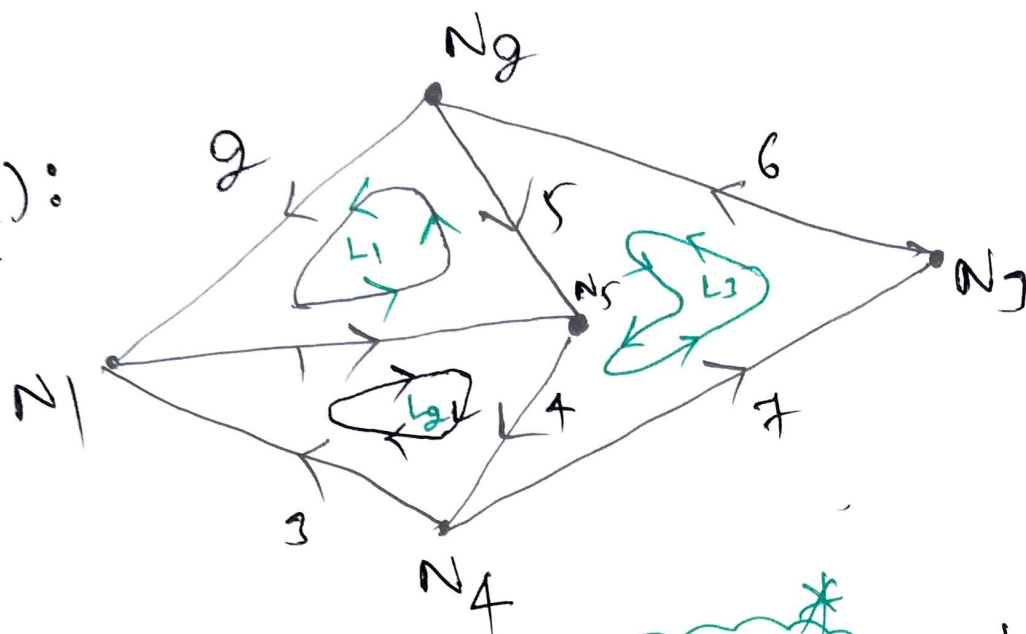

Each of the  $e$  edge currents can be expressed as a linear combination of  $K$  quantities,  $i_{L1}(t)$ ,  $i_{L2}(t)$ , ...,  $i_{LK}(t)$  known as loop currents which represent the current flowing in  $K$  independent circuits.


The edge current vector (the currents flowing through the edges at a given time) can be expressed as LOOP current vector

as

$$i(t) = B_f^T i_L(t)$$

Where  $B_f$  is the fundamental circuit matrix.

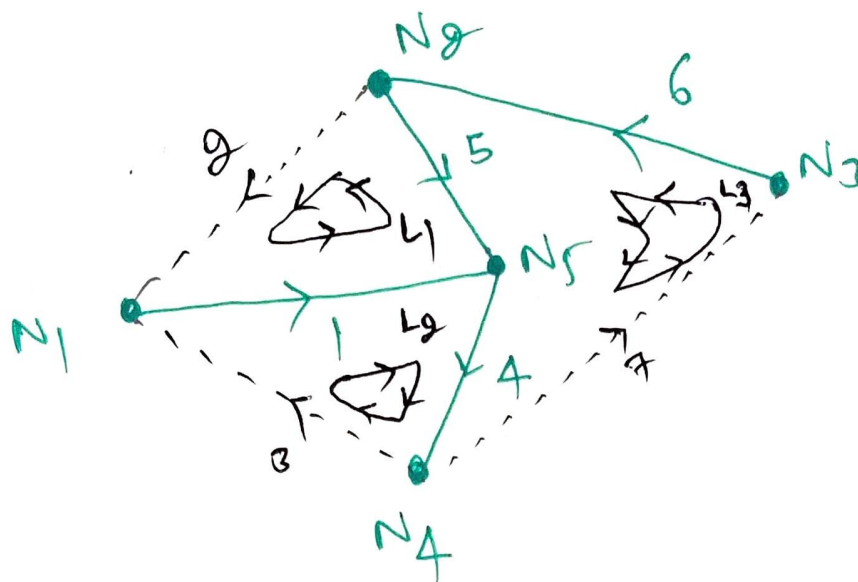consider a spanning ~~di-graph~~ ~~of fig(1)~~ tree from the digraph given in fig(1)



$$B_f = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 \end{matrix} \\ \begin{matrix} L_1 \\ L_2 \\ L_3 \end{matrix} & \begin{bmatrix} 1 & 1 & 0 & 0 & -1 & 0 & 0 \\ 1 & 0 & 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 1 & 1 & 1 \end{bmatrix} \end{matrix}$$

The edge current vector in terms  
of loop-current vector is

$$i(t) = B_f^T i_L(t)$$

$$\begin{bmatrix} i_1(t) \\ i_2(t) \\ i_3(t) \\ i_4(t) \\ i_5(t) \\ i_6(t) \\ i_7(t) \end{bmatrix} = \begin{bmatrix} 1 & 1 & 0 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 1 & 1 \\ -1 & 0 & 1 \\ 0 & 0 & 1 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_{L1}(t) \\ i_{L2}(t) \\ i_{L3}(t) \end{bmatrix}$$

ex:  $i_1(t) = i_{L1}(t) + i_{L2}(t)$

## \*\* Edge voltage in terms of node voltage \*\*

The edge voltage in terms of the node voltage are given by

$$V(t) = A_f^T V_N(t)$$

related to a reference vertex

where  $A_f$  is reduced incidence matrix.

(Refer Narsing Rao)